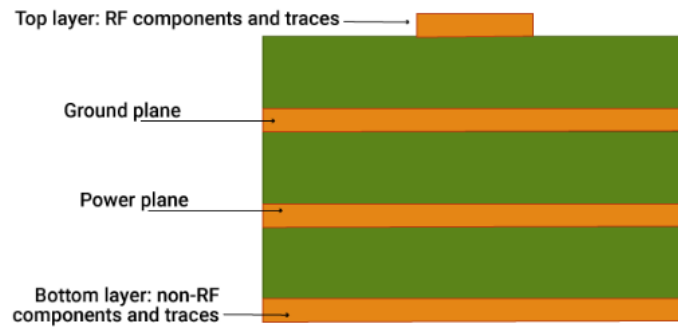




# PCB Design

## Layer



Dielectric constant for FR4-grade : 4.5

## Transmission line (Microstrip trace)

### *Transmission line effects*

There is no straightforward answer to the question “when do I have to start considering transmission line properties?” The best response is, when the effects become important to you. One of the simplest electrical laws is that which relates frequency, wavelength and the speed of light:

$$\lambda = 3 \cdot 10^8 / f$$

which is modified because of the reduction in velocity of propagation when a (lossless) dielectric medium is involved by the relative permittivity or dielectric constant of the medium,


$$\lambda_d = \lambda / \sqrt{\epsilon_r}$$

One rule of thumb is that a cable should be considered as a transmission line when the wavelength of the highest frequency carried is less than ten times its length. You may be embarrassed by transmission line effects at lengths of one fortieth the wavelength or

---

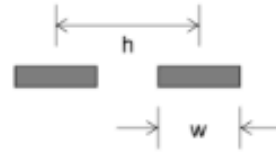**1. Side-by-side parallel strip**


$$Z_0 = 120/\sqrt{\epsilon_r} \cdot \ln \{h/w + \sqrt{[(h/w)^2 - 1]}\}$$



---

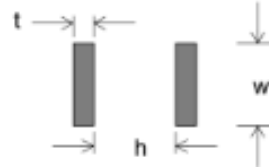**2. Face-to-face parallel strip**

$$Z_0 = \begin{matrix} 377/\sqrt{\epsilon_r} \cdot h/w & \text{if } h > 3t, w \gg h \\ 120/\sqrt{\epsilon_r} \cdot \ln 4h/w & \text{if } h \gg w \end{matrix}$$



---

**3. Parallel wire**

$$Z_0 = \begin{matrix} 120/\sqrt{\epsilon_r} \cdot \ln \{h/d + \sqrt{[(h/d)^2 - 1]}\} \\ 120/\sqrt{\epsilon_r} \cdot \ln 2h/d & \text{if } d \ll h \end{matrix}$$




( $Z_0$  of typical pvc-insulated pairs and twisted pairs is around 100Ω)

---

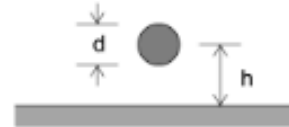**4. Wire parallel to infinite plate**


$$Z_0 = \begin{matrix} 60/\sqrt{\epsilon_r} \cdot \ln \{2h/d + \sqrt{[(2h/d)^2 - 1]}\} \\ 60/\sqrt{\epsilon_r} \cdot \ln 4h/d & \text{if } d \ll h \end{matrix}$$



---

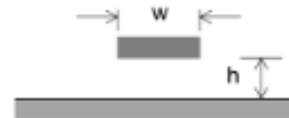**5. Strip parallel to infinite plate**

$$Z_0 = \begin{matrix} 377/\sqrt{\epsilon_r} \cdot h/w & \text{if } w > 3h \\ 60/\sqrt{\epsilon_r} \cdot \ln 8h/w & \text{if } h > 3w \end{matrix}$$



---

**6. Coaxial**

$$Z_0 = 60/\sqrt{\epsilon_r} \cdot \ln (D/d)$$



Dielectric constants of various materials	$\epsilon_r$	Velocity factor ( $1/\sqrt{\epsilon_r}$ )
Air	1.0	1.0
Polythene/Polyethylene	2.3	0.66
PTFE	2.1	0.69
Silicone Rubber	3.1	0.57
FR4 Fibreglass PCB	4.5 (typ)	0.47
PVC	5.0	0.45

**Table 1.9** Characteristic impedance, geometry and dielectric constants

## Passive Component for RF circuit

SRF (Self Resonance Frequency) : Maximum Frequency that can use before the component transform to Invalid behavior


### *Recommended Maximum Frequencies for Capacitors*

TYPE	MAX FREQUENCY
Aluminum Electrolytic	100 kHz
Tantalum Electrolytic	1 MHz
Mica	500 MHz
Ceramic	1 GHz

# LC Ladder Bandpass Filter (@436MHz)
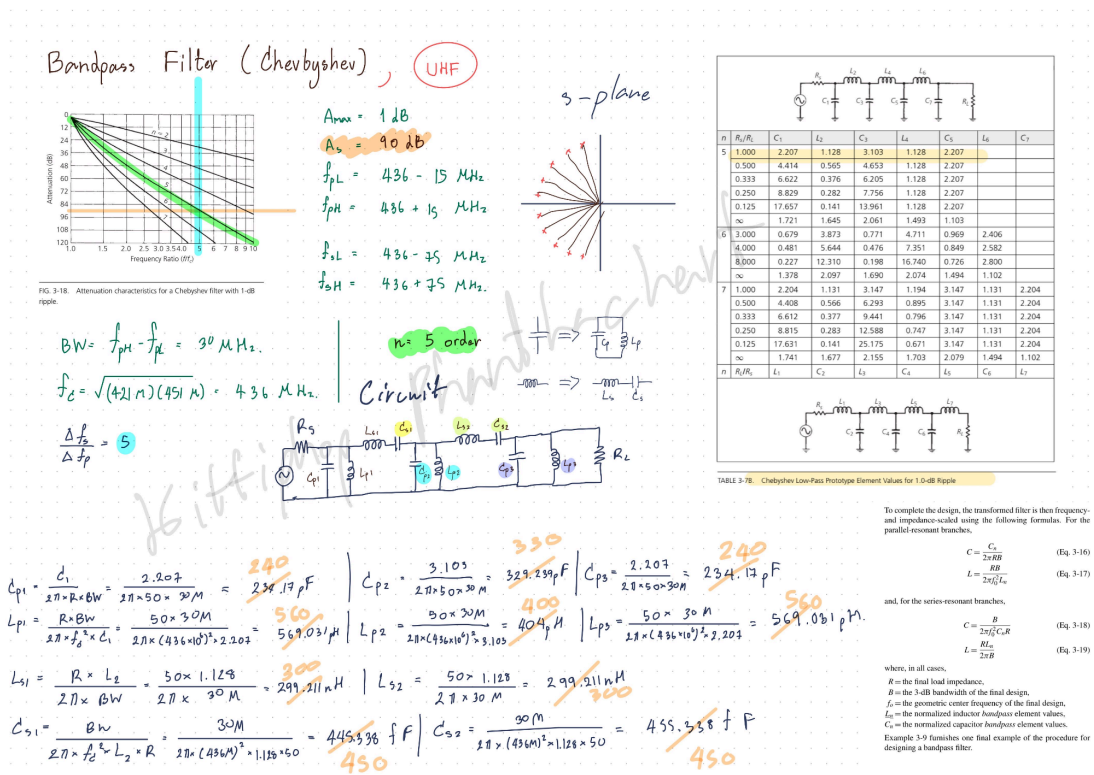
## LC Ladder Bandpass Filter Design

Type of Filter : 5<sup>th</sup> order Chebyshev filter with 1-dB Ripple



## Reference Filter Design :

PDF RF Circuit Design - 2nd Edition.pdf / Chapter 3 FILTER Design



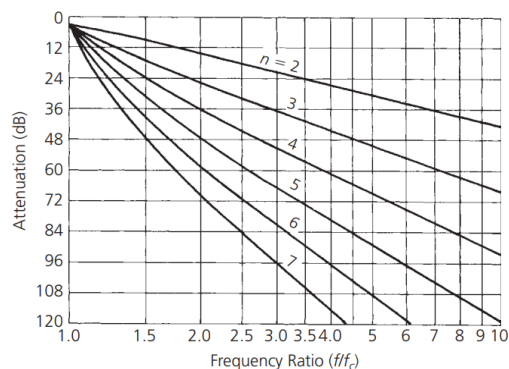


FIG. 3-18. Attenuation characteristics for a Chebyshev filter with 1-dB ripple.

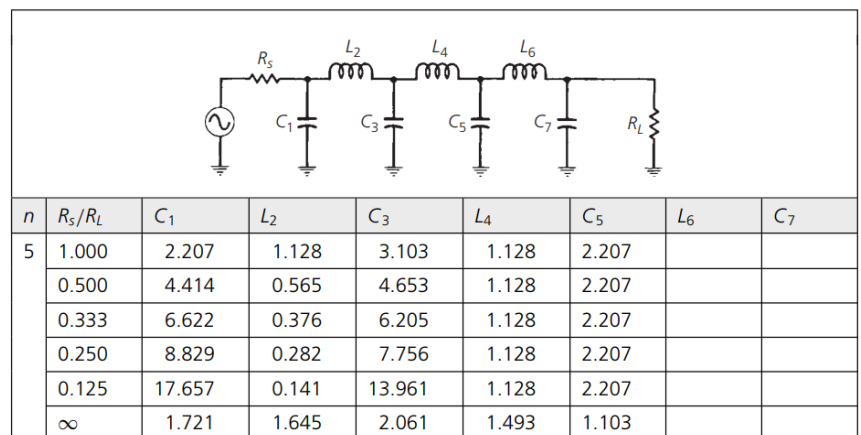

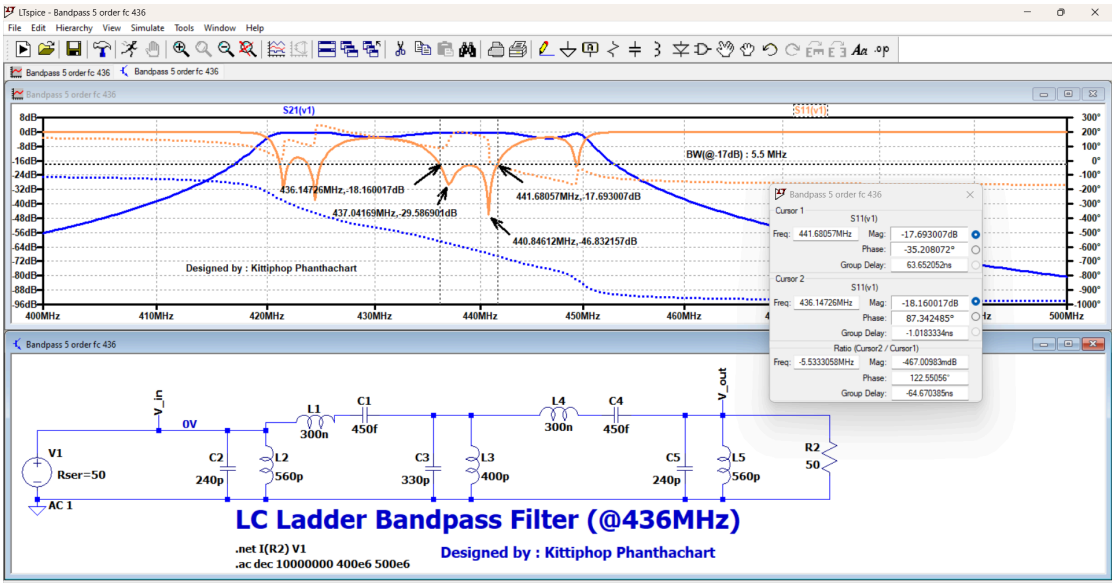
# LC Ladder Bandpass Filter Simulation



By LTspice : [Bandpass 5 order fc 436MHz.asc](#)





# LC Ladder Bandpass Filter Schematic

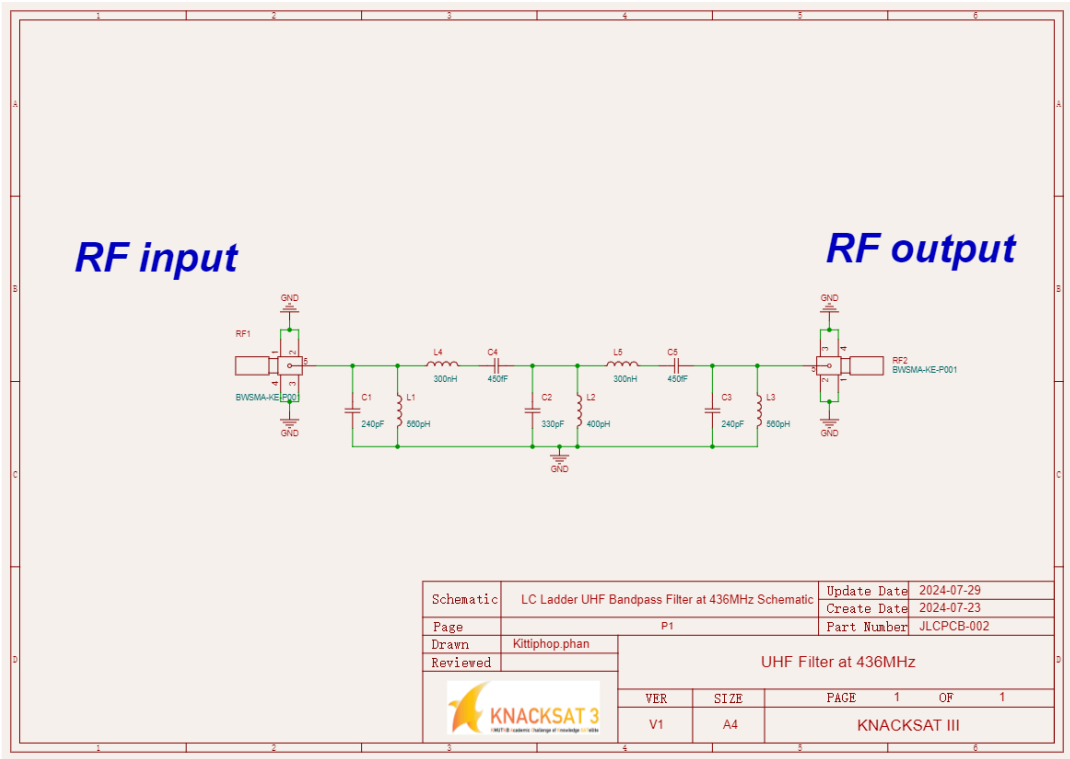

# LC Ladder Bandpass Filter PCB Design

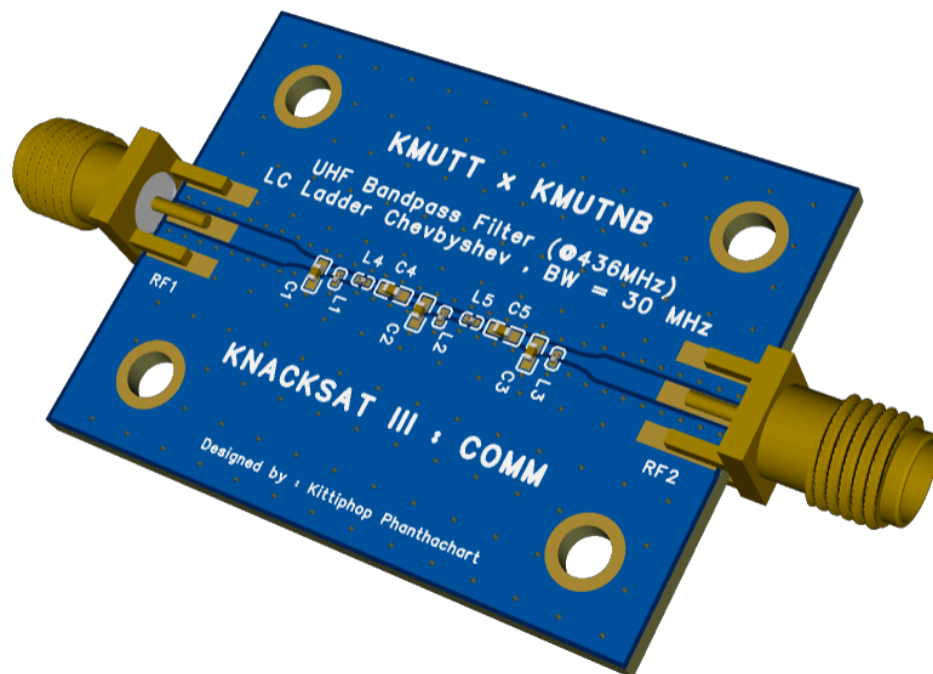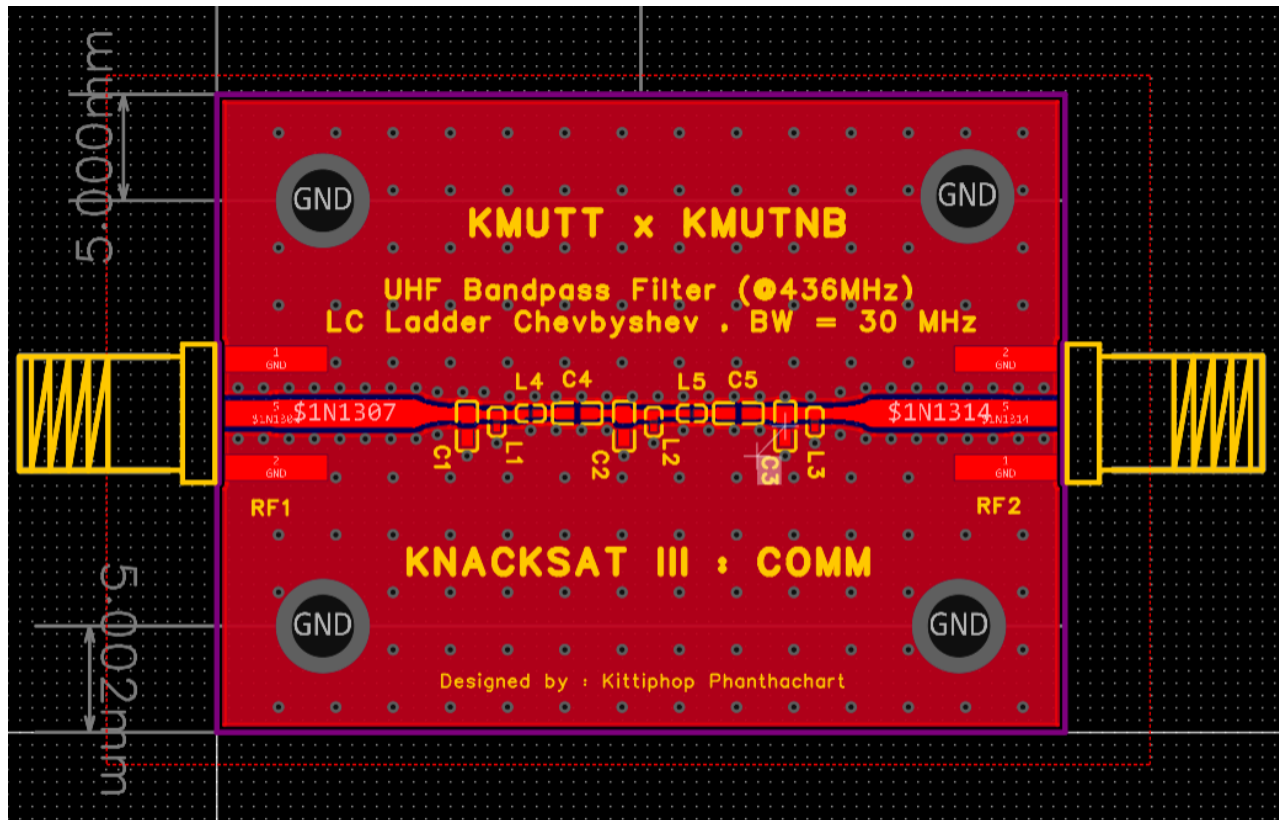
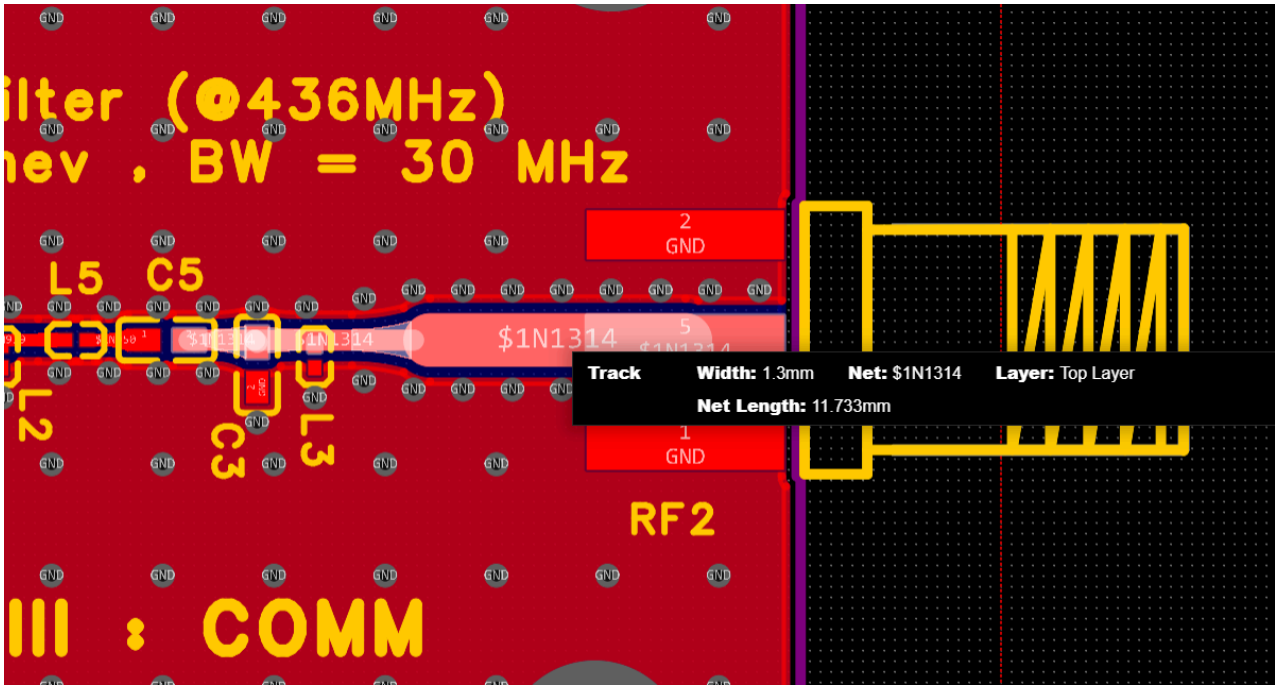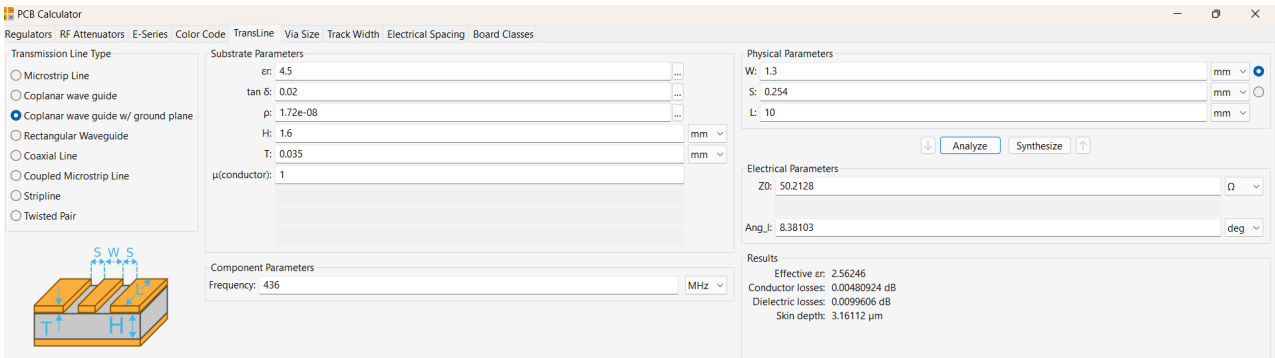
# Microstrip Transmission Line Calculated



$Z_0 = 50.2128 \text{ Ohms}$